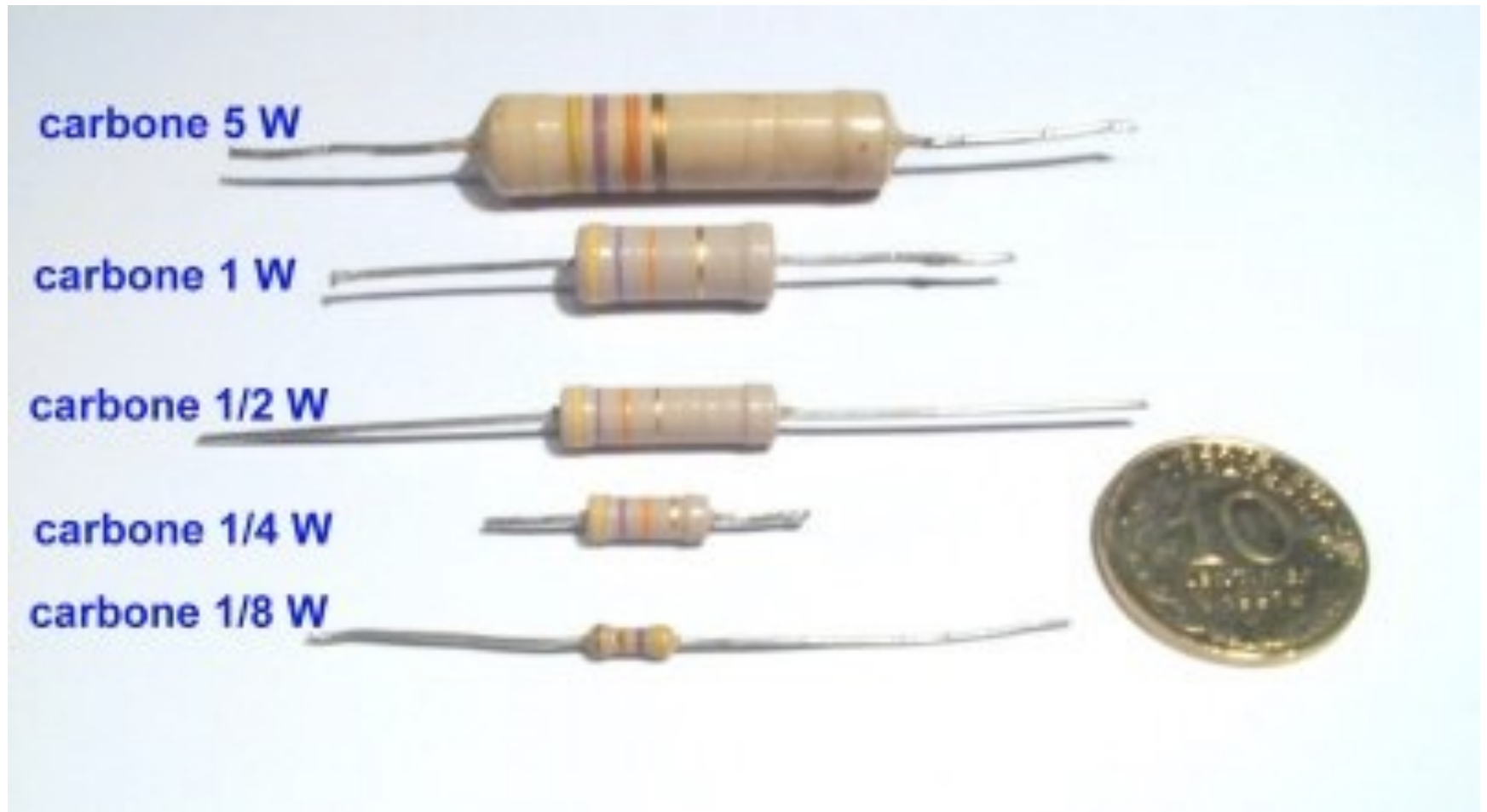


Notions of electronics





Pierre Rossel

Resistor



Resistor

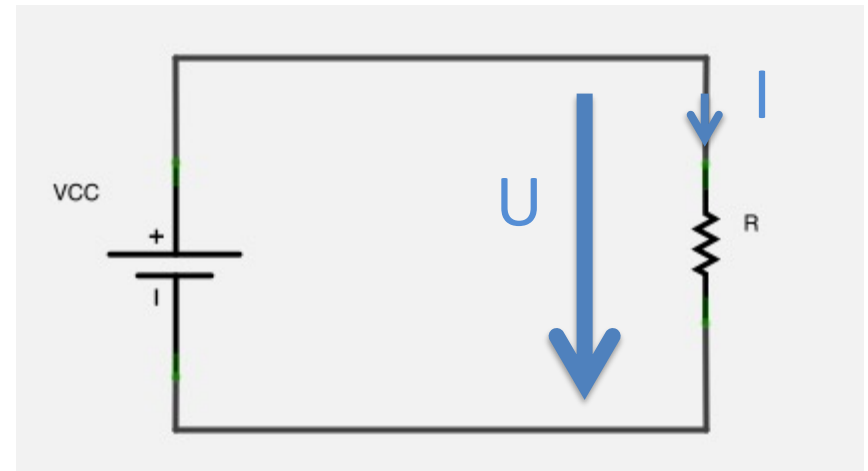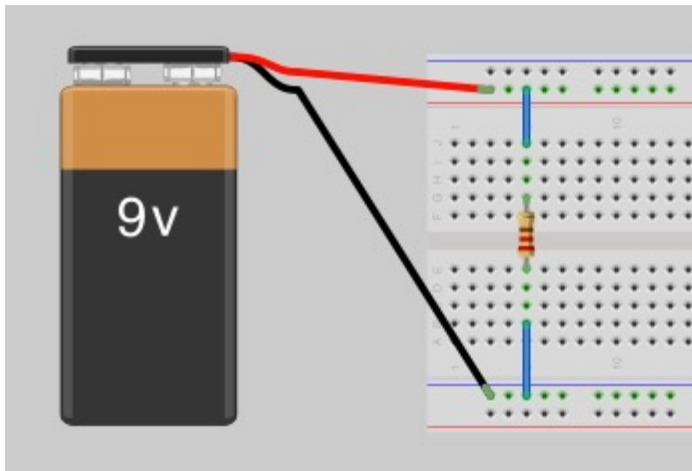


- A voltage across a resistor causes a current
- The higher the voltage, the higher the current
- The higher the resistance, the lower the current

Resistor

- Units and symbols

Element	Unit	Symbol	Name in schematics
Voltage	Volt	[V]	U or V
Resistance	Ohm	[Ω] or [ohm]	R
Current	Ampere	[A]	I

Resistor

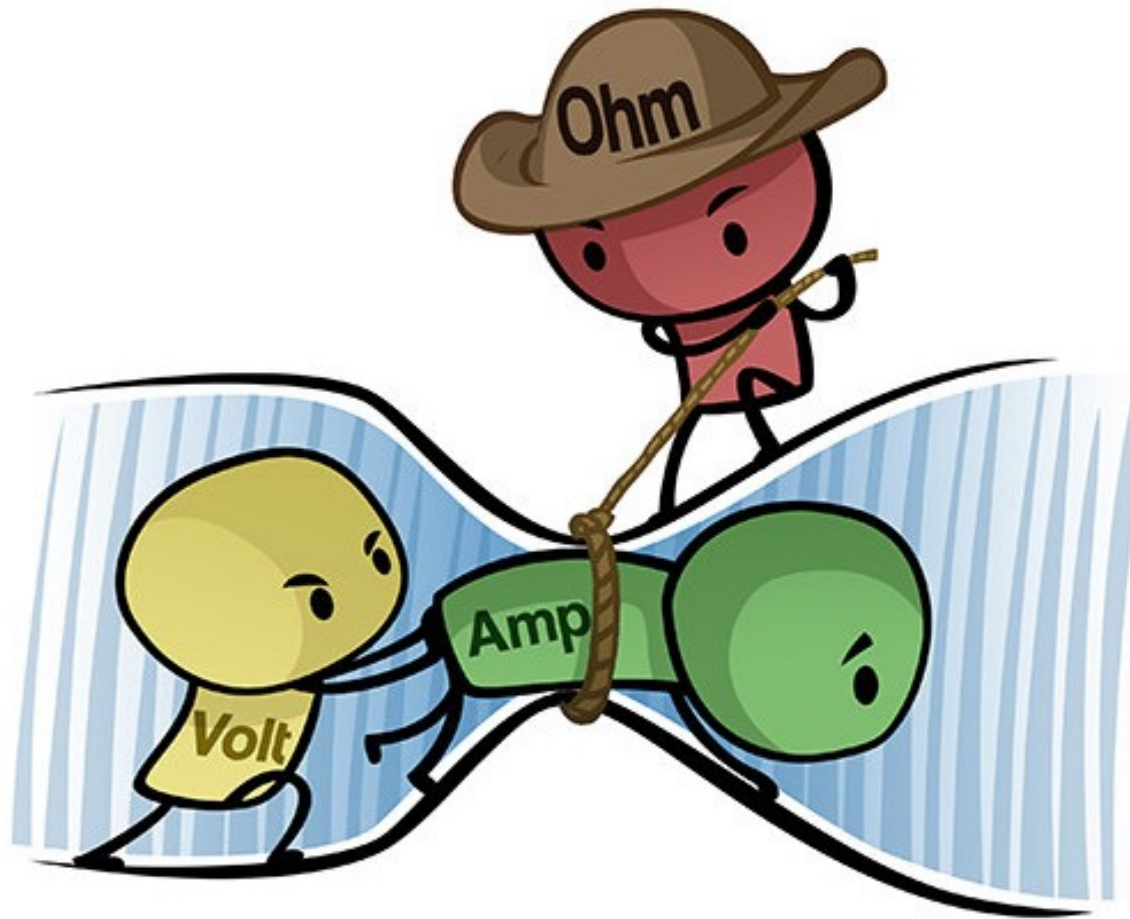

Resistor

Open circuit


- Infinite resistance
- Zero current: the current does not flow

Short circuit

- Zero resistance
- Infinite current (theoretically, but not in practice because the resistance is never really zero, even in a copper wire)


Measuring a voltage

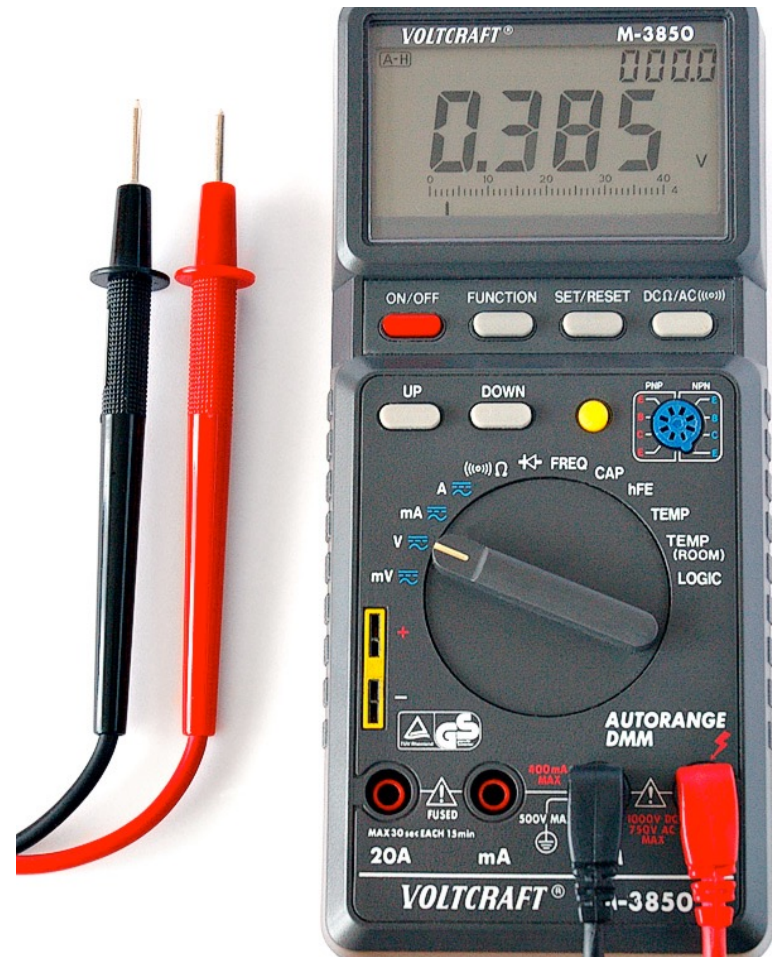- Using a voltmeter or a multimeter configured as a voltmeter
- High resistance
- Low current
- Parallel connection
- Little risk, a weak current flows through the instrument



Ohm's law

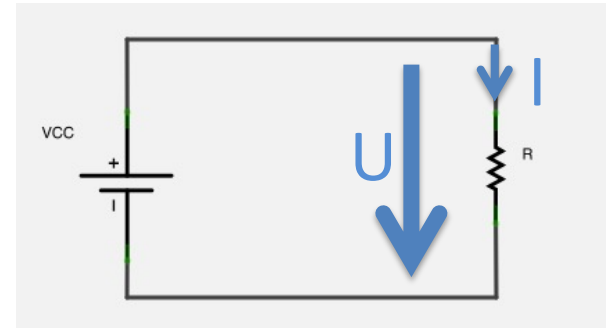- Voltage
 - Name: U
 - Unit: volt
 - Symbol: [V]
- Current
 - Name: I
 - Unit: ampere
 - Symbol: [A]
- Resistance
 - Name: R
 - Unit: ohm
 - Symbol: [Ω] or [ohm].



$$U_{[V]} = R_{[\Omega]} \cdot I_{[A]}$$

$$I_{[A]} = \frac{U_{[V]}}{R_{[\Omega]}}$$

$$R_{[\Omega]} = \frac{U_{[V]}}{I_{[A]}}$$

Calculation of current 1

- On a 12 V battery, we connect a bulb with a resistance of 12 Ω .
 - Draw the diagram.
 - Calculate the current.
-
- $I = U / R$
 - $I = 12 \text{ [V]} / 12 \text{ [\Omega]}$
 - $I = 1 \text{ [A]}$

Current calculation 2



- On a 12 V battery, we power a bulb that is 220 Ω .
- Draw the diagram
- Calculate the current

- $I = U / R$
- $I = 12 \text{ [V]} / 220 \text{ [\Omega]}$
- $I = 0.0545 \text{ [A]}$
- $I = 54.5 \text{ [mA]}$

Resistance calculation

- I want a voltage of 2.5 V at the terminal of a resistor to limit the current to 10 mA.
- What resistance value should I choose?
- $R = U / I$
- $R = 2.5 \text{ [V]} / 0.010 \text{ [A]}$
- $R = 250 \text{ } [\Omega]$

Color code

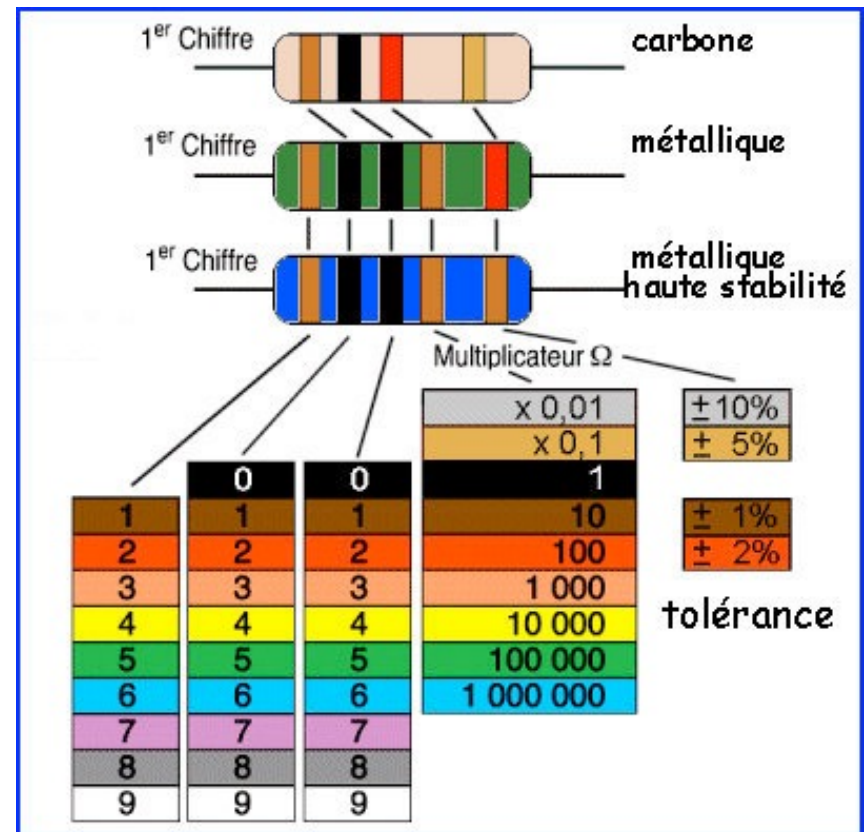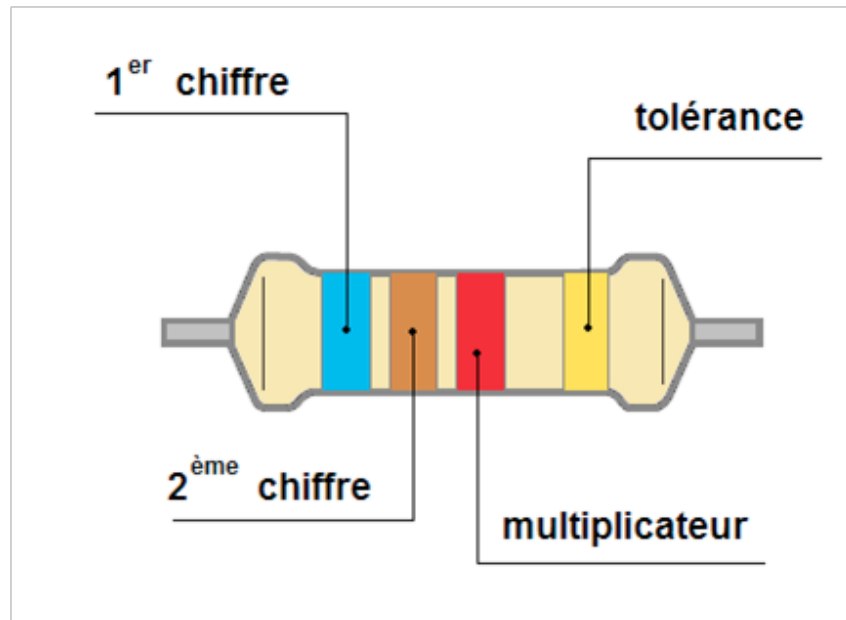

Power

- Joule effect
 - A resistor through which a current flows consumes a certain amount of electrical energy and transforms it into heat
- Power
 - Name: P
 - Unit: Watt
 - Symbol: [W]



$$P = U \cdot I$$

$$P = R \cdot I^2$$

$$P = \frac{U^2}{R}$$

Power calculation 1

- On a 12 V battery, we connect a bulb with a resistance of 12 Ω .
- Draw the diagram
- Calculate the power dissipated by the bulb

- $P = U^2 / R$
- $P = 12^2 / 12$
- $P = 12 \text{ [W]}$

Power calculation 2


- On a 12 V battery, we power a 220 Ω bulb.
- Draw the diagram
- Calculate the power dissipated by the bulb

- $P = U^2 / R$
- $P = 12^2 / 220$
- $P = 0.65 \text{ [W]}$

Power calculation 3

- On a 12 V battery, we connect a 60 Watt bulb
- Draw the diagram
- Calculate the current flowing through the bulb
- $P = U * I$
- $I = P / U$
- $I = 60 / 12 = 5 \text{ [A]}$

Voltage divider

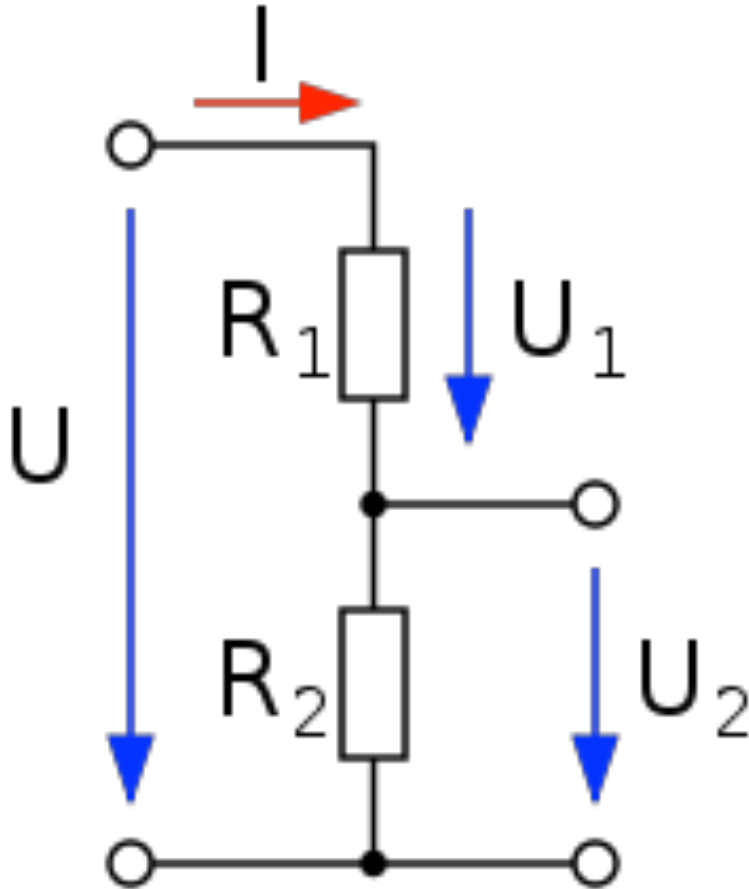

- In series, the voltages add up

$$U = U_1 + U_2$$

- The current through the two resistors is the same

$$U_1 = R_1 * I$$

$$U_2 = R_2 * I$$

$$U = (R_1 + R_2) * I$$

Calculation of a divisor 1

- From a 5 V voltage source, I want to have a 5 mA current through a 330 Ω resistor. To do this, I decide to add a resistor in series.
- Draw the diagram
- Calculate the value of the additional resistance
- $U_2 = R * I = 330 * 0.005 = 1.65 \text{ V}$
- $U_1 = U - U_2 = 5 - 1.65 = 3.35 \text{ V}$
- $R_1 = U_1 / I = 3.35 \text{ V} / 0.005 \text{ A} = 670 \Omega$

Calculation of a divisor 2


- Using a voltage divider, I want to go from 12 V to 4 V across a 1 k Ω resistor (R2)
- Draw the diagram and calculate R1
- $I = U_2 / R_2 = 4 \text{ V} / 1000 \text{ } \Omega = 0.004 \text{ A}$
- $U_1 = U - U_2 = 12 - 4 = 8 \text{ V}$
- $R_1 = U_1 / I = 8 \text{ V} / 0.004 \text{ A} = 2000 \text{ } \Omega = 2 \text{ k}\Omega$

LED (Light-Emitting Diode)


LED (Light Emitting Diode)



LED

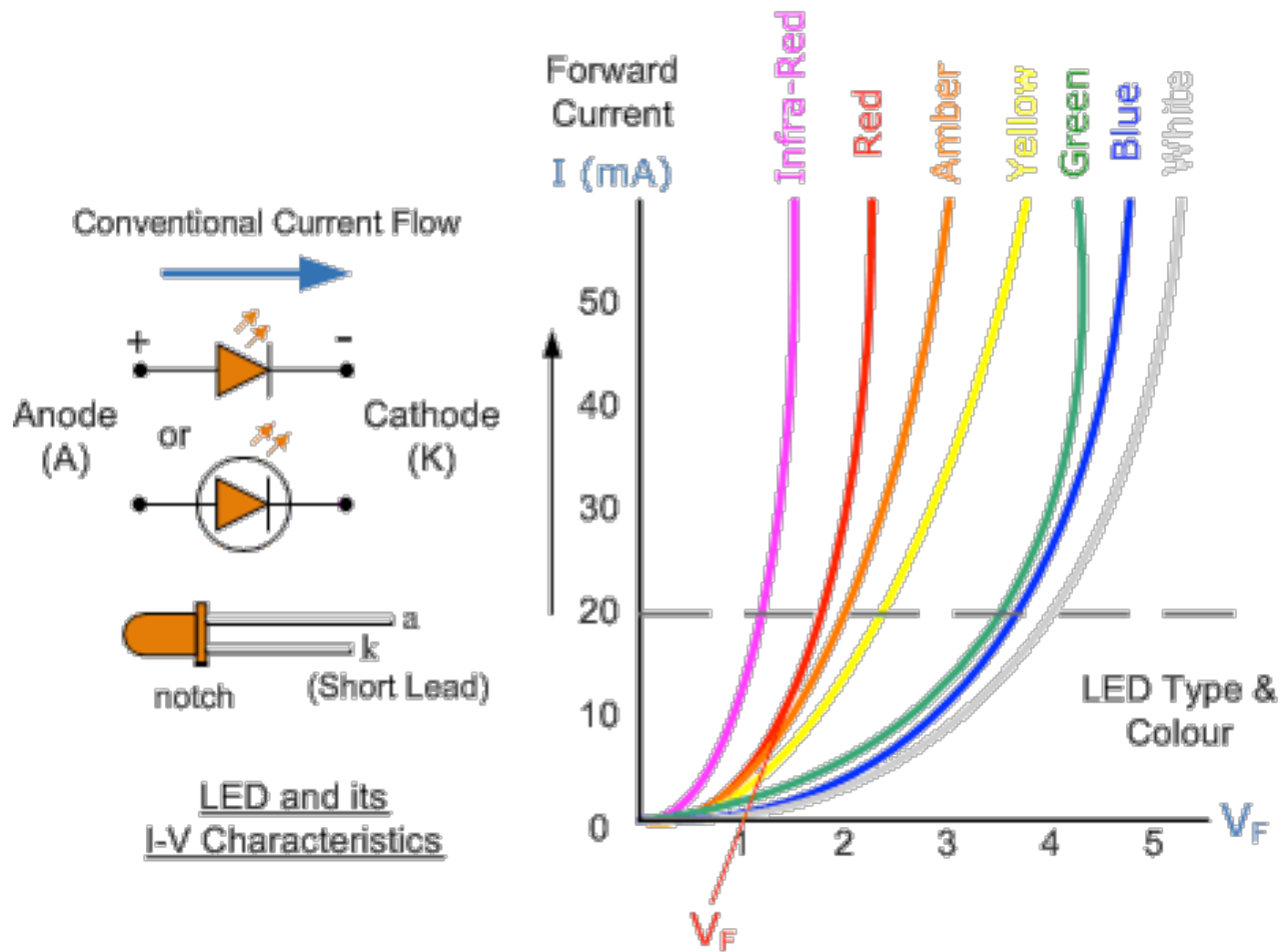

Resistance calculation for LED

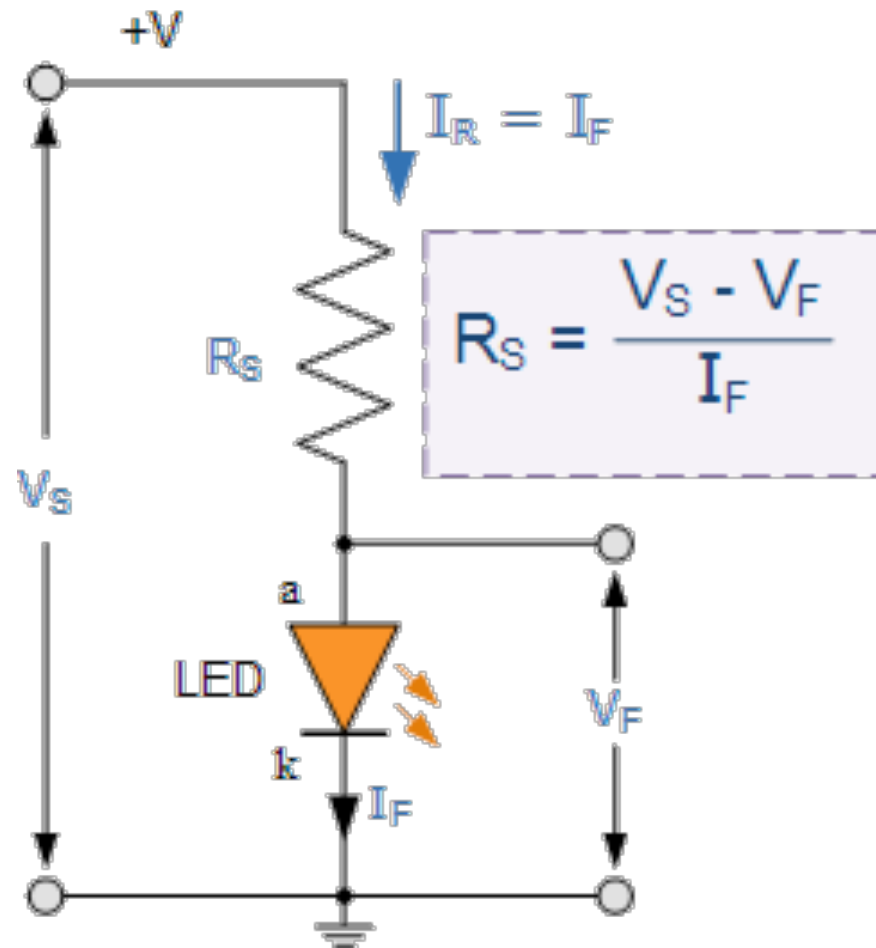

Resistance calculation for LED

- Using a 12 V battery, I want to power an LED that has a voltage drop of 3 V with a current of 20 mA.
- What value of resistor should I put in series with it?
- $U_{\text{(resistance)}} = 12\text{V} - 3\text{V} = 9\text{ V}$
- $R = U / I = 9\text{ V} / 0.020\text{ A}$
- $R = 450\ \Omega$